

Current Electricity — CBSE Pattern Test 1

Class 12 Physics · 90 minutes · 40 marks · Sections A–D with answer key · Narayan Gurukul Academy

Test 1 — CBSE Pattern (90 minutes, 40 marks)

Class 12 Physics · Current Electricity · Narayan Gurukul Academy (ClassApna)

General Instructions: (1) This paper has four sections — Section A (1×10), Section B (2×4), Section C (3×4) and Section D (5×2) — total 40 marks. Time allowed: 90 minutes.

(2) All questions are compulsory. No overall choice is given; internal choice, where allowed, is clearly marked.

(3) For MCQ questions choose the single correct option; for VSA answers write a single line.

(4) Take $g = 10 \text{ m/s}^2$. All symbols carry their usual meaning. Use of a calculator is not permitted.

Section A — MCQ & VSA ($10 \times 1 = 10$ marks)

- The ratio of the maximum to the minimum effective resistance obtainable with n identical resistors of resistance R is
 - n^2
 - n
 - $1/n$
 - n^3
- A current of 5 A flows through a wire for 2 minutes. The charge that crosses any section of the wire is
 - 600 C
 - 10 C
 - 0.04 C
 - 300 C
- Ohm's law asserts that
 - for a conductor at constant temperature the plot of I versus V is linear, i.e. R is independent of V
 - $R = V/I$ for every device at every instant
 - R is always constant for any material
 - I is directly proportional to R
- The equivalent resistance of 1Ω , 2Ω and 3Ω connected in parallel is
 - $6/11 \Omega$
 - 6Ω
 - $11/6 \Omega$
 - $1/6 \Omega$
- Kirchhoff's junction rule is based on the conservation of
 - charge
 - energy
 - linear momentum
 - magnetic flux
- For a metallic conductor, the temperature coefficient of resistance is typically
 - positive
 - negative
 - zero
 - infinite
- State Ohm's law for a metallic conductor.
- Define current density and write its SI unit.

9. State Kirchhoff's loop rule for a closed circuit.
10. Write the relation between the drift velocity v_d of free electrons, the current I , the area of cross-section A and the free-electron number density n of a wire.

Section B — Short Answer I ($4 \times 2 = 8$ marks)

11. A copper wire of area of cross-section $2.0 \times 10^{-6} \text{ m}^2$ carries a steady current of 3.0 A. If the free-electron number density is $8.5 \times 10^{28} \text{ m}^{-3}$, find the drift velocity of the free electrons.
12. At room temperature (27.0°C) the resistance of a heating element is 100Ω . What is the temperature of the element if its resistance is found to be 117Ω ? The temperature coefficient of resistance of the material is $1.70 \times 10^{-4} ^\circ \text{C}^{-1}$.
13. Three resistors 2Ω , 4Ω and 5Ω are combined in parallel and connected to a battery of emf 20 V and negligible internal resistance. Determine the current through each resistor and the total current drawn from the battery.
14. At a junction of a network, currents of 3 A and 4 A enter the node while a current of 2 A leaves it along one branch. Find the current leaving the node along the remaining branch, stating the rule you use.

Section C — Short Answer II ($4 \times 3 = 12$ marks)

15. Derive the relation $I = n A e v_d$ for the current in a conductor in terms of free-electron density n , drift velocity v_d and area A .
16. Given three resistors 1Ω , 2Ω and 3Ω , how would you combine them to obtain an equivalent resistance of (i) $11/3 \Omega$ and (ii) $11/5 \Omega$?
17. A cell of emf 4 V and internal resistance 2Ω is connected in parallel with a cell of emf 2 V and internal resistance 2Ω , with like terminals joined through a 6Ω resistor. Using Kirchhoff's laws, find the current in the 6Ω resistor.
18. A battery of emf 10 V and internal resistance 3Ω is connected to a resistor; the current in the circuit is 0.5 A. Find the resistance of the resistor and the terminal voltage of the battery when the circuit is closed.

Section D — Long Answers ($2 \times 5 = 10$ marks)

19. (a) State Kirchhoff's junction rule and loop rule, and name the conservation principle underlying each. (b) Derive the balance condition $P/Q = R/S$ of a Wheatstone bridge using Kirchhoff's laws.
20. (a) Show that the effective resistance of two resistors R_1 and R_2 connected in parallel is smaller than the smaller of the two. (b) A wire of resistance 12Ω is bent into the form of a closed square. Find the resistance between two diagonally opposite corners of the square.

Answer Key (Marking Scheme)

- Q1 – (A) n^2 (series nR , parallel R/n). Q2 – (A) 600 C ($Q = 5 \times 120$). Q3 – (A). Q4 – (A) $6/11 \Omega$ ($1/(1+1/2+1/3)$). Q5 – (A) charge. Q6 – (A) positive (metals).
- Q7 – V I at constant temperature ($R = V/I$ constant). Q8 – $j = I/A$, SI unit A/m^2 . Q9 – In any closed loop, the algebraic sum of the emfs and potential drops is zero ($\sum \mathcal{E} - \sum IR = 0$). Q10 – $I = n A e v_d$.
- Q11 – $v_d = I/(nAe) = 3.0/(8.5 \times 10^{28} \times 2.0 \times 10^{-6} \times 1.6 \times 10^{-19}) \approx 1.1 \times 10^{-4} \text{ m/s}$. Q12 – $R/R_0 = 1 + \alpha \Delta t$ $\Delta t = (17/100)/(1.70 \times 10^{-4}) = 1000^\circ \text{C}$ $\Theta = 1027^\circ \text{C}$.
- Q13 – $R_{eq} = 20/19 \Omega$; currents 10 A (2Ω), 5 A (4Ω), 4 A (5Ω); total 19 A. Q14 – Junction rule (charge conservation): $I = 3 + 4 - 2 = 5 \text{ A}$.
- Q15 – In time dt charge $nA v_d e dt$ crosses a section $\Phi = nA e v_d$ (full micro derivation accepted). Q16 – (i) (1Ω $\parallel$ 3Ω) + 3Ω : $2/3 + 3 = 11/3 \Omega$; (ii) (2Ω $\parallel$ 3Ω) + 1Ω : $6/5 + 1 = 11/5 \Omega$.

Q17 – Branch equations $4 - 2I_1 = 2 - 2I_2$ and $4 - 2I_1 = 6(I_1 + I_2)$ give $I_1 = 5/7$ A, $I_2 = -2/7$ A. $\Rightarrow \Omega = 3/7 \approx 0.43$ A. Q18 – $R + r = \epsilon/I = 20 \Omega$ $\Rightarrow = 17 \Omega$; $V = \epsilon - Ir = 10 - 1.5 = 8.5$ V.

Q19 – (a) Junction rule $\Rightarrow$ Conservation of charge; loop rule $\Rightarrow$ Conservation of energy. (b) At balance $I_G = 0$: $P/Q = R/S$ (standard derivation). Q20 – (a) $1/R_{eq} = 1/R_1 + 1/R_2$ $\Rightarrow R_{eq} = R_1 R_2 / (R_1 + R_2) < \min(R_1, R_2)$. (b) Each side 3Ω ; between opposite corners $(3+3) \parallel (3+3) = 6 \parallel 6 = 3 \Omega$.