

Current Electricity — CBSE Pattern Test 2

Class 12 Physics · 90 minutes · 40 marks · Sections A–D with answer key · Narayan Gurukul Academy

Test 2 — CBSE Pattern (90 minutes, 40 marks)

Class 12 Physics · Current Electricity · Narayan Gurukul Academy (ClassApna)

General Instructions: (1) This paper has four sections — Section A (1×10), Section B (2×4), Section C (3×4) and Section D (5×2) — total 40 marks. Time allowed: 90 minutes.

(2) All questions are compulsory. No overall choice is given; internal choice, where allowed, is clearly marked.

(3) For MCQ questions choose the single correct option; for VSA answers write a single line.

(4) Take $g = 10 \text{ m/s}^2$. All symbols carry their usual meaning. Use of a calculator is not permitted.

Section A — MCQ & VSA ($10 \times 1 = 10$ marks)

- The balance condition of a Wheatstone bridge with arms P, Q, R, S in cyclic order is
 - $P/Q = R/S$
 - $P \cdot R = Q \cdot S$
 - $P + Q = R + S$
 - $P = Q = R = S$
- A galvanometer of resistance G giving full-scale deflection for current I_g is shunted with a resistance S. The range of the resulting ammeter is
 - $I_g(1 + G/S)$
 - $I_g(1 + S/G)$
 - $I_g G/S$
 - $I_g/(G + S)$
- While discharging, the terminal voltage V of a cell of emf ϵ and internal resistance r carrying a current I is
 - $V = \epsilon - I r$
 - $V = \epsilon + I r$
 - $V = \epsilon$
 - $V = I r - \epsilon$
- In a potentiometer, two cells of emfs ϵ_1 and ϵ_2 give balance lengths l_1 and l_2 on the same wire. The ratio ϵ_1/ϵ_2 equals
 - l_1/l_2
 - l_2/l_1
 - $l_1 l_2$
 - $l_1 - l_2$
- In a metre bridge experiment the balance point is at 39.5 cm when the resistor S in the right gap is 12.5Ω . The unknown resistance R is
 - 8.2Ω
 - 12.5Ω
 - 4.7Ω
 - 20.5Ω
- For a cell whose balance length is l_1 in open circuit and l_2 with a shunt R in its external circuit, the internal resistance r is
 - $r = (l_1/l_2 - 1) R$
 - $r = (l_2/l_1 - 1) R$
 - $r = (l_1 - l_2) R$
 - $r = (l_1 + l_2) R/l_1$

7. State the balance condition of a metre bridge in terms of the two gap resistances and the ratio of the two wire lengths.
8. Why must an ammeter have a very low resistance?
9. Why are the connecting strips of a metre bridge made of thick copper?
10. What is a balance point in a potentiometer experiment?

Section B — Short Answer I ($4 \times 2 = 8$ marks)

11. A galvanometer of resistance $20\ \Omega$ gives full-scale deflection for a current of $10\ \text{mA}$. Find the shunt resistance needed to convert it into an ammeter of range $0\text{--}5\ \text{A}$.
12. The same galvanometer ($20\ \Omega$, $10\ \text{mA}$) is to be converted into a voltmeter of range $0\text{--}50\ \text{V}$. Find the resistance that must be connected in series with it.
13. In a metre bridge experiment the balance point shifts from $39.5\ \text{cm}$ to $60.5\ \text{cm}$ when the resistors R and S are interchanged. If $S = 12.5\ \Omega$, find R .
14. Six lead-acid secondary cells, each of emf $2.0\ \text{V}$ and internal resistance $0.015\ \Omega$, are joined in series to supply a resistance of $8.5\ \Omega$. Find the current drawn from the supply and its terminal voltage.

Section C — Short Answer II ($4 \times 3 = 12$ marks)

15. Describe how a galvanometer is converted into an ammeter and derive the expression $S = I_g G / (I - I_g)$ for the shunt resistance.
16. Derive the balance condition $P/Q = R/S$ of a Wheatstone bridge using Kirchhoff's laws.
17. A galvanometer of resistance $30\ \Omega$ gives full-scale deflection for a current of $2\ \text{mA}$. Find (i) the shunt needed to measure currents up to $2\ \text{A}$ and (ii) the series resistance needed to measure voltages up to $2\ \text{V}$.
18. A potentiometer is used to compare the emfs of two cells: a cell of emf $1.25\ \text{V}$ balances at a length of $35.0\ \text{cm}$, and the second cell balances at $63.0\ \text{cm}$. Find the emf of the second cell.

Section D — Long Answers ($2 \times 5 = 10$ marks)

19. (a) Describe, with a labelled circuit diagram, how a potentiometer is used to determine the internal resistance of a cell, and derive the formula $r = (l_1/l_2 - 1) R$. (b) A $1.5\ \text{V}$ cell gives a balance point at $76.3\ \text{cm}$ in open circuit and at $64.8\ \text{cm}$ when a resistor of $9.5\ \Omega$ is connected across it. Determine the internal resistance of the cell.
20. (a) Why is the galvanometer in a potentiometer more accurate than a voltmeter for measuring the emf of a cell? (b) Determine the current in each branch of the network of Fig 3.30 ($AB = 10\ \Omega$, $BC = 5\ \Omega$, $CD = 10\ \Omega$, $DA = 5\ \Omega$, $BD = 5\ \Omega$) connected to a $10\ \text{V}$ battery in series with a $10\ \Omega$ resistor across A–C.

Answer Key (Marking Scheme)

- Q1 – (A) $P/Q = R/S$. Q2 – (A) $I_g(1 + G/S)$. Q3 – (A) $V = \epsilon - I r$. Q4 – (A) I_1/I_2 . Q5 – (A) $8.2\ \Omega$. Q6 – (A) $r = (l_1/l_2 - 1) R$. Q7 – $R/S = l/(100 - l)$. Q8 – An ammeter is connected in series; a large resistance would alter the current it measures. Q9 – Thick copper strips keep the (unaccounted) connection resistance negligible in the bridge formula. Q10 – The jockey position where the galvanometer shows zero deflection; the cell then draws no current.
- Q11 – $S = (0.010 \times 20)/(5 - 0.010) = 0.20/4.99 \approx 0.04\ \Omega$. Q12 – $R = 50/0.010 - 20 = 4980\ \Omega$. Q13 – $R = 12.5 \times 39.5/60.5 = 8.2\ \Omega$. Q14 – $\epsilon = 12\ \text{V}$, $r = 0.09\ \Omega$: $I = 12/8.59 = 1.4\ \text{A}$; $V = I \times 8.5 = 11.9\ \text{V}$.
- Q15 – Shunt in parallel draws $(I - I_g)$; equal p.d. $\Rightarrow I_g G = (I - I_g) S \Rightarrow I_g G / (I - I_g)$. Q16 – At balance $I_G = 0$, potential division gives $P/Q = R/S$. Q17 – (i) $S = (0.002 \times 30)/(2 - 0.002) = 0.030\ \Omega$; (ii) $R = 2/0.002 - 30 = 970\ \Omega$. Q18 – $\epsilon_2 = 1.25 \times 63.0/35.0 = 2.25\ \text{V}$.

Q19 – (a) Standard set-up + derivation (see note); (b) $r = (76.3/64.8 - 1) \times 9.5 = 1.685 \approx 1.7 \, \Omega$. Q20 – (a) At balance the cell draws no current, so the true emf is measured (a voltmeter draws a finite current and reads $V = \varepsilon - I r$). (b) Branch currents: $AB = 4/17 \, \text{A}$, $BC = 6/17 \, \text{A}$, $CD = -4/17 \, \text{A}$, $DA = 6/17 \, \text{A}$, $BD = -2/17 \, \text{A}$; total = $10/17 \, \text{A}$.